

داخل سیستم fsm توسط ماژول xnor comparator برابری passed data و پسورد چک شده و داخل وایر p1 ذخیره میشود وایر p2 هم $\sim p1$ است. به عنوان رجیستر از سه تا دی فلیپ فلاپ استفاده شده که طبق کد نوشته شده از خط ۳۱ تا ۵۲ ورودی ها و خروجی های دی فلیپ فلاپ ها مقداردهی شدند. خروجی های دی فلیپ فلاپ ها که q0 و q1 و q2 هستند داخل دو جعبه ی odd و even که دوتا and هستند استفاده میشود و خروجی even enable که نشان دهنده این هست که اطلاعات داخل جعبه زوج ذخیره شده باشند یک and هست که مقدار q2 و $q1 \sim$ و q3 بعلاوه ریکوئست کانفیرم و مقدار نات ورودی d تعیین میشود. جعبه odd خروجی فرد است توسط and مقادیر q2 و $q1 \sim$ و q3 آتش و ریکوئست و کانفیرم و خود مقدار دی تعیین میشود. داخل محیط شبیه سازی به مقادیر ورودی یک حالت پایه داده شده که passed data ۱۰۱۰ هست و پسورد اولیه غلط و ۱۰۰۰ است و مقدار دی و ۰۰۰۱ و مقدار کلاک کانفیرم و ریکوئست هم صفر است. کلاک به تعداد ۳۰ بار در دوره های ۱۰ نانو ثانیه تغییر میکند و مقادیر هم پس از ۲۰ نانو ثانیه تغییر میکنند تا حالات مختلف را ببینیم. در نهایت هم در جدول زمانی یک حالت نمایش داده شده است.

```

21 module DFF(input clk,input q,output q2);
22     //a DFlipFlop by data flow design
23     reg q2;
24     always @ ( posedge clk ) begin
25         q2 <= q;
26     end
27 endmodule

```

```

21 module xnorComparator4bit(input [3:0] first,input [3:0] second,output out);
22     wire [3:0] result;
23     xnor
24         b0 (result[0], first[0], second[0]),
25         b1 (result[1], first[1], second[1]),
26         b2 (result[2], first[2], second[2]),
27         b3 (result[3], first[3], second[3]);
28
29     and finalResult (out, result[3], result[2], result[1], result[0]);
30
31 endmodule
32

```

```

21 module FSM(input [3:0] passedData,input clk,input confirm,input request,input [3:0] password,input d
22 ,output evenEnable,output oddEnable);
23 //The FSM circuit which will manage the user inputs,and change the outputs if needed.Using 3 D-FFs and 1 comparator.
24
25 // The password comparator
26 wire p1, p2;
27 xnorComparator4bit checkingPassword (passedData, password, p1);
28 not pInventor (p2, p1);
29
30
31 // FlipFlops inputs and outputs
32 wire q0, q02, q1, q12, q2, q22, in0, in1, in2;
33 not
34     Inventor0 (q02, q0),
35     Inventor1 (q12, q1),
36     Inventor2 (q22, q2);
37
38 // N2 Flip Flop input
39 wire n2MiddleWire;
40 or n2Middle (n2MiddleWire, q2, confirm);
41 and n2Input (in2, q0, q12, request, n2MiddleWire);
42
43 // N1 Flip Flop input
44 wire n1MiddleWire;
45 or n1Middle (n1MiddleWire, q2, p2);
46
47 // N0 Flip Flop input
48 wire n0MiddleWire1, n0MiddleWire2, CP;
49 not cInventor (CP, confirm);
50 and n0Middle1 (n0MiddleWire1, q0, CP);
51 or n0Middle2 (n0MiddleWire2, q22, n0MiddleWire1);
52 and n0Input (in0, q12, request, n0MiddleWire2);
53
54
55 // Flip Flops instantiates
56 DFF
57     n0 (clk, in0, q0),
58     n1 (clk, in1, q1),
59     n3 (clk, in2, q2);
60
61
62 // Output functions
63 wire dp;
64 not dInventor (dp, d);
65 and
66     evenOut (evenEnable, q2, q12, q0, request, confirm, dp),
67     oddOut (oddEnable, q2, q12, q0, request, confirm, d);
68 endmodule

```

```

50
51 initial begin
52     // Clock initialize
53     clk = 0;
54     repeat (30)
55         #10 clk = ~ clk;
56 end
57
58 initial begin
59     // Initialize Inputs
60     passedData = 4'b1010;
61     clk = 0;
62     confirm = 0;
63     request = 0;
64     password = 4'b1000;
65     d = 4'b0001;
66
67     // Wait 100 ns for global reset to finish
68     #100;
69
70     // Add stimulus here
71     // Defining a process
72     # 10
73     request = 1;
74     # 20
75     confirm = 1;
76     # 20
77     confirm = 1;
78     # 20
79     request = 0;
80     confirm = 0;
81     # 20
82     password = 4'b1010;
83     request = 1;
84     confirm = 1;
85     # 20
86     d = 4'b0000;
87     confirm = 1;
88     # 20
89     request = 0;
90     confirm = 0;
91     # 20
92     password = 4'b1010;
93     request = 1;
94     confirm = 1;
95     # 20
96     d = 4'b0011;
97     confirm = 0;
98     # 20
99     request = 0;
100
101     confirm = 0;
102     # 20
103     password = 4'b1010;
104     request = 1;
105     confirm = 1;
106     # 20
107     d = 4'b0011;
108     confirm = 1;
109     # 20
110     request = 0;
111     $finish;

```

